



TECHNICAL UNIVERSITY OF MOMBASA
INSTITUTE OF COMPUTING AND INFORMATICS

UNIVERSITY EXAMINATION FOR:
BBIT/SEP2019/J-FT, BTIT/AUG2021/S-PT
CCI 4202: ELECTRONICS

PAPER 2

SPECIAL/SUPPLEMENTARY EXAMINATION

SERIES: MARCH 2022

TIME: 2HOURS

DATE: Pick DateDec2021

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **FIVE** questions. Attempt question ONE (Compulsory) and any other TWO questions.

Do not write on the question paper.

Question ONE

- a) Explain any TWO application of Resistors in an electronic circuit. 2 Marks

Capacitor and Inductors are passive electronic components that have a lot of applications in electronics either as alone or together in a circuit. **REQUIRED**

- b) Describe any FOUR types of Inductors. 4 Marks
c) Describe any FOUR application of Capacitors. 4 Marks

Semiconductors form the bulky of active electronic components that form the backbone of electronic devices that drive most modern electronics circuits.

- d) Distinguish between PIN and Avalanche diodes with the aid of a sketch. 4 Marks
e) Explain two major application of transistors. 2 Marks
f) Explain the THREE symbol for the Field Effect Transistors with aid of a sketch. 3 Marks
g) Explain the FIVE idealized characteristics of Operational Amplifier OP Amp. 5 Marks

- h) Transistors are commonly used as amplifiers, there are several classes of amplifiers that have different power efficiencies, with the aid of a sketch describe any THREE classes of amplifier.

6 Marks

Question TWO

The Field Effect Transistor FET have a narrow "Channel" of N-type or P-type silicon with electrical connections at either end commonly called the DRAIN and the SOURCE respectively.

- a) Explain the advantages of FET over BJT

2 Marks

Show the biasing arrangement the following FETs with the aid of a sketch.

- b) Depletion-mode N-Channel junction FET

3 Marks

- c) Depletion-mode N-Channel MOSFET

3 Marks

- d) Enhancement-mode N-Channel MOSFET

3 Marks

Show the output characteristic voltage-current curves with the aid of a sketch of:

- e) Junction FET

3 Marks

- f) Depletion-mode N-Channel MOSFET

3 Marks

- g) Enhancement-mode N-Channel MOSFET

3 Marks

Question THREE

A semiconductor PN junction diode have lots of application in Electronics, however they must be biased before being put in to meaningful application.

- a) Show how the biasing is achieved in a PN junction diode with the aid of a sketch. 3 Marks
- b) Draw a well labeled I/V characteristics of PN junction diode biasing. 5 Marks
- c) Describe at least SIX types of diodes commonly used in electronic circuits. 12 Marks

Question FOUR

The word Transistor is an acronym, and is a combination of the words Transfer Varistor used to describe their mode of operation way back in their early days of development.

- a) With the aid of sketch show the symbol, construction and analogy of BJT transistors.

5 Marks

- b) Discuss the following BJT transistors is configuration with the aid of a sketch.

i. Common Base.

5 Marks

ii. Common Emitter.

5 Marks

iii. Common Collector or Emitter Follower.

5 Marks

The diagram shows a circuit with two voltage sources, V_1 and V_2 , and three resistors, R_1 , R_2 , and R_3 . V_1 is on the left, V_2 is on the right, and R_2 is in the center. R_1 is on the top wire between V_1 and R_2 , and R_3 is on the top wire between R_2 and V_2 . The bottom wire connects the negative terminals of V_1 and V_2 . Numerous handwritten red annotations are present: $6A$ and $3A$ near V_1 ; 1.99 and $3A$ near R_1 ; $6A$ and $6A$ near R_2 ; $3A$ and $2A$ near R_3 ; and $3A$ and $3A$ near V_2 . Some annotations are crossed out or scribbled over.

$$18 \times 4 = 72$$

Using the diagram 1.1 above, find

- 6 Marks
5 Marks
5 Marks
4 Marks

$$\begin{array}{r} 4 \times 6 + 120 \\ \hline 10 \end{array}$$

$$\frac{144}{10}$$

$$\frac{72 \times 10}{144} = 5A$$

$$\frac{12 \times 6 + 72}{18}$$

$$4 + 4 = 8$$

$$\frac{48}{800} = 6A$$